

## Appendix A Exercises

**A.1** [10] ⟨A.2⟩ In addition to the basic laws we discussed in this section, there are two important theorems, called DeMorgan's theorems:

$$\overline{A + B} = \overline{A} \cdot \overline{B} \text{ and } \overline{A \cdot B} = \overline{A} + \overline{B}$$

Prove DeMorgan's theorems with a truth table of the form:

$A$	$B$	$\overline{A}$	$\overline{B}$	$\overline{A + B}$	$\overline{A \cdot B}$	$\overline{A} \cdot \overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1	1	1	1
0	1	1	0	0	0	1	1
1	0	0	1	0	0	1	1
1	1	0	0	0	0	0	0

Table 1: DeMorgan's Theorems

The table above is given in the text. Note that columns  $\overline{A + B}$  and  $\overline{A} \cdot \overline{B}$  contain the same values and  $\overline{A \cdot B}$  and columns  $\overline{A} + \overline{B}$  also contain the same values, thus proving DeMorgan's Theorems.

**A.3** [10] ⟨A.2⟩ Show that there are  $2^n$  entries in a truth table for a function with  $n$  inputs.

Let boolean function  $f$  with  $n$  inputs be written as:

$$f(x_1, x_2, \dots, x_{n-1}, x_n)$$

Each input  $x_i$  can take on one of two values, 0 or 1. The total number of input combinations is given by the product of the possibilities for each of the  $n$  inputs:

$$\prod_{i=1}^n 2 = 2 \times 2 \times \dots \times 2 \times 2 = 2^n$$

Therefore, the number of different input combinations is  $2^n$ , and since each row in a truth table corresponds to one unique combination of inputs, there are  $2^n$  entries in a truth table for a function with  $n$  inputs.

Example where  $n = 3$ :

	$x_1$	$x_2$	$x_3$
<b>1</b>	0	0	0
<b>2</b>	0	0	1
<b>3</b>	0	1	0
<b>4</b>	0	1	1
<b>5</b>	1	0	0
<b>6</b>	1	0	1
<b>7</b>	1	1	0
<b>8</b>	1	1	1

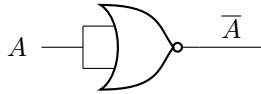
Table 2: Truth table with  $n = 3$  inputs

Table contains  $2^3 = 8$  rows.


**A.5** [15] ⟨A.2⟩ Prove that the NOR gate is universal by showing how to build the AND, OR, and NOT functions using a two-input NOR gate.

<b>a</b>	<b>b</b>	<b>NOR</b>
0	0	1
0	1	0
1	0	0
1	1	0


Table 3: NOR gate

**NOT**

By the truth table for a NOR gate (Table 3), when both inputs  $A$  and  $B$  are 0, the output is 1, and when both inputs are 1, the output is 0. This behavior mirrors that of a NOT operation. A NOT gate can therefore be created by connecting both inputs of a NOR gate.

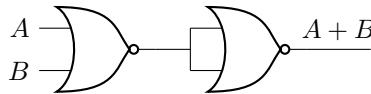**OR**

The NOR gate produces the inverse of the OR operation. By applying a NOT operation (constructed using NOR gates) to the output of a NOR gate, the OR operation is implemented.

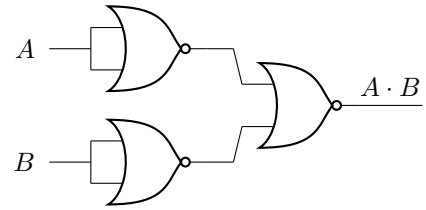**AND**

$$\overline{\overline{A} + \overline{B}} = \overline{\overline{A}} \cdot \overline{\overline{B}} = A \cdot B$$

By DeMorgan's Theorem ( $\overline{A \cdot B} = \overline{A} + \overline{B}$ )

**A.7** [10] ⟨A.2, A.3⟩ Construct the truth table for a four-input odd-parity function (see page A-65 for a description of parity).

<b>A</b>	<b>B</b>	<b>C</b>	<b>D</b>	<b>Parity</b>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Table 4: Four-input odd-parity function

**A.17** [5] (A.2, A.3) Show a truth table for a multiplexor (inputs A, B, and S; output C), using don't cares to simplify the table where possible.

A	B	S	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Table 5: 2-1 MUX

A	B	S	C
0	X	0	0
X	0	1	0
1	X	0	1
X	1	1	1

Table 6: 2-1 MUX with  
don't cares

S	C
0	A
1	B

Table 7: 2-1 MUX simplified